

OIA Lab 1: Introduction to ELVIS Virtual Instrumentation

BIOE 385 Bioinstrumentation Laboratory

Goals

1. Become familiar with the NI-ELVIS Setup and Virtual Instrumentation
2. Perform simple analysis of practical DC circuits using ELVIS
3. Investigate the behavior of an RC circuit

Textbook Readings

Note: these readings will help you with your project. You are responsible for knowing this information before next lab although these should be a review.

- 7.1: Safety
- 2.1-3: Theory of Electronics, Electric Current and Voltage
- 2.9-12: Wire Gauges, Grounds, Electric Circuits, Ohm's Law and Resistors
- 2.14: Measuring Voltage, Current and Resistance
- 2.16: Open and Short Circuits

Part 1: ELVIS Orientation

Introduction

The system you will be working with in the labs for this course is called ELVIS and was developed by [National Instruments \(NI\)](#). ELVIS stands for Educational Laboratory Virtual Instrumentation Suite. A virtual instrument (VI) is essentially a software representation of a physical instrument. In the study of circuits, we commonly use three instruments – function generators, oscilloscopes and power supplies. The ELVIS system can recreate the functions of these instruments on the computer, thus simplifying our bench setup.

The ELVIS system uses software to replicate:

- **A function generator** - an instrument capable of producing periodic voltage waveforms (e.g. sine waves, square waves, triangular waves), at different frequencies and amplitudes. It is used to provide voltage input to test the output response of a circuit.
- **An oscilloscope** - an electronic instrument that graphically displays a measured voltage (y-axis) as a function of time (x-axis). For example, the oscilloscope will be used to display the output from a function generator in part two of this lab.

- A **variable power supply** - an instrument that is used as a source of potential difference for use in circuitry, (e.g. to provide a DC voltage).
- A **digital multi-meter (DMM)** - an instrument that is used to measure two or more electrical values - often times voltage (volts), current (amps) and resistance (ohms).

This software can also be used to perform useful functions such as creating a **bode plot** of the frequency response of a circuit.

The first time you run ELVIS you will need to perform a self-calibration. You might also want to do this periodically to improve the accuracy of your system - in order to compensate for inherent sources of error commonly found on electronic components, such as nonlinearities and drift due to time and temperature.


Getting Started

The NI ELVIS II Series Prototyping Board (protoboard) connects to the workstation and provides an area for building electronic circuitry.



Warning: Always ensure that the prototyping board power switch is off before inserting or removing it from the workstation.

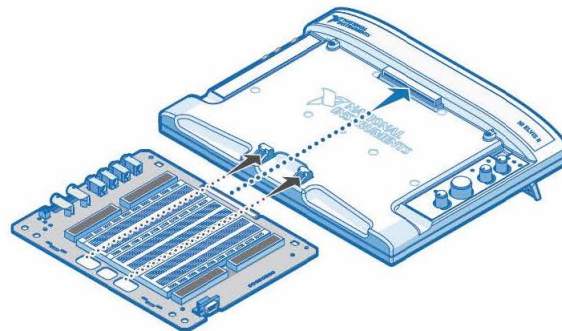
1. Install your **NI ELVIS Protoboard** on top of the ELVIS II unit – make sure it is properly aligned at the front and back and push until you hear a click. *Tip: use one hand to hold the back of the unit, while you use the other hand to push the protoboard in place.*



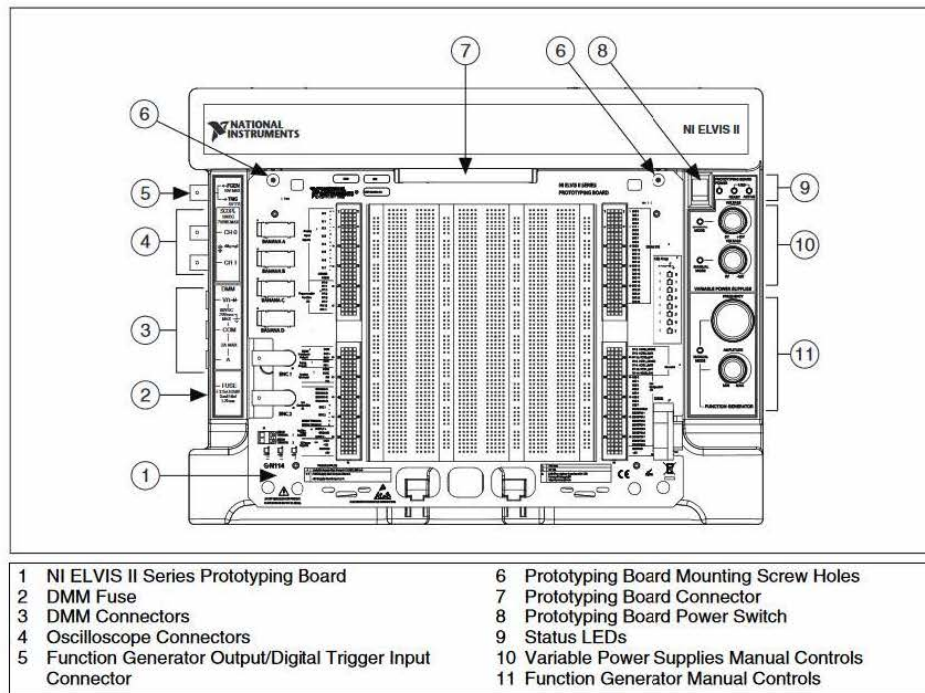2. Turn on your ELVIS unit's system power – this is located on the back panel of the unit. The orange **USB READY** LED indicator on the front panel should now be lit.
3. Turn on the prototyping board power switch located on the top of the unit (see diagram). The green **PROTOTYPING BOARD POWER** LED should now be lit.

Self-calibration Routine

Always perform this step with the prototyping board power ON. Step-by-step instructions are as follows:



1. Double-click on the NI MAX icon on the desktop. If the icon is not present, follow Start → Programs → Applications → National Instruments → NI ELVISmx for NII ELVIS & NI myDAQ → NI ELVISmx Instrument Launcher.
2. Under Resources, double click Measurement and Automation Explorer.
3. Expand the My System → Devices and Interfaces → NI ELVIS II “Dev1”.
4. Click on NI ELVIS II “Dev1”.
5. Click on Self Test and wait for the “The self test completed successfully” message.
6. Next, click on Self-Calibrate and wait for the operation to continue.
7. Close the Test Panel window and you are ready to continue to the next step.

Introduction to ELVIS

1. Double-click on the NI ELVIS Instrument Launcher icon found on the desktop. If the icon is not present, follow Start → Programs → Applications → National Instruments → NI ELVISmx for NI ELVIS & NI myDAQ → NI ELVISmx Instrument Launcher.
2. From the Instruments & Apps menu, select the Oscilloscope option. The NI-ELVIS virtual instrument oscilloscope is capable of reading signals from the built-in ELVIS SCOPE (ch0 and ch1) or from circuits on the protoboard (AI 0 thru AI 7).
 - (a) The NI ELVIS oscilloscope can display signals from the Analog Input Channels (AI 0-7) located in your protoboard.
 - (b) Connect a wire from the function generator output to the analog input channel 0+ and ground the AI0- channel directly using AIGND. Make sure the oscilloscope source is the same channel as the one you are feeding your signal to. *A general safety guideline is to make connections while the prototype board power is off.*

- (c) Click Run (you will not see your signal yet; continue to next step).
3. From the Instruments & Apps menu, choose the Function Generator option and click on Manual Mode. Generate a signal using the manual controls (these are found on the ELVIS II unit's front panel) for the function generator. The manual mode LED should be ON. If you want to control the function generator with the ELVIS software, unclick Manual Mode on your virtual instrument (controlled via computer).
 - (a) Turn on Manual Mode.
 - (b) On the ELVIS unit's function generator panel, select the sine wave signal option
 - (c) Using the knobs on the ELVIS unit, adjust the frequency to 500 Hz, and turn the amplitude to 3/4 of the maximum setting (indicator should be pointing right).
 - (d) On the oscilloscope screen, notice that you can see the root-mean-squared (RMS) amplitude, frequency, and peak-to-peak amplitude (Vp-p) of the input signal displayed. What exactly do these parameters refer to?
 - (e) Adjust the oscilloscope vertical scale such that the signal height (peak to peak) covers approximately 2 squares. What is your vertical scale?
 - (f) Adjust the timebase. What is happening to your signal? Select a value that results in a few cycles of your signal displayed on screen.
 4. Does your signal appear stable on oscilloscope screen?
 5. Have an instructor or TA check your answers and show them your signal.

Triggers are used to stabilize signals viewed using oscilloscopes. They function by ensuring that the horizontal sweep (signal reading) always begins at the same point of a repeating signal, resulting in a clear picture. The most common type of triggering is edge triggering, where the sweep begins when the input signal rises or falls past a certain voltage level. The ELVIS system has a built-in function for edge triggering that is synchronized with the signal being generated by the function generator.

1. Select EDGE for the type on the trigger menu and Chan 0 for your source. What happens to your signal?
2. You are now looking at your triggered signal. Experiment by adjusting the amplitude and frequency controls on the ELVIS unit. Change the slope, level and horizontal positions. How do these changes affect the triggered signal? Describe how you think the trigger is working.
3. Select Run Once under Acquisition Mode on the Oscilloscope screen. Describe the difference between this option and using a trigger signal.
4. Return to Run Continuously and click the Log button to save the data for the sweep as a txt (text) file. Open the file and understand how your data has been recorded.
5. The previous section used the function generator built into the ELVIS unit. Now generate a signal using the virtual instrument function generator.
 - (a) Open the Function Generator from the ELVIS menu. *At this point, you must switch the manual control of the ELVIS unit function generator off.*
 - (b) Turn on the virtual instrument function generator and select a triangular waveform with 500 Hz frequency and set the peak amplitude to 2.0 V (4Vpp).

- (c) Adjust your oscilloscope display to show 5 cycles starting and ending at the highest point (signal should look like: VVVVV). Each cycle should cover 2 squares vertically and 2 squares horizontally. Write down the values you used to achieve this.
- (d) Adjust the DC offset of your signal and describe what happens.
- (e) Show your signal (described above) to an instructor or TA.

Introduction to the ELVIS Prototyping board

1. Identify the 5 individual protoboards within the full ELVIS protoboard. The protoboards on the far left and far right each contain four columns of pin sockets. Each row on these left and right protoboards is connected to the main ELVIS unit or the connectors on the protoboard, to send/receive signals to/from these locations, and are grouped according to their function. For example, locate the group of pin sockets labeled Function Generator (FUNC_OUT). Within this group, all the rows deliver the same waveform from the function generator (ELVIS unit front panel or virtual instrument), that we previously displayed on the virtual oscilloscope screen. **IMPORTANT:** All four pin sockets in each row are connected together to the terminal labeled on the protoboard. For example, all four pin sockets in the +5 V row are at a potential of +5 V. All four pin sockets in the GROUND row are at a potential of 0 V.
2. Locate the rows of four pin sockets at +5 V and Ground. Use a wire to connect one of the +5 V pins to a pin for any one of the group of 8 LEDs (on the right side of your protoboard). Use a second wire to light any other LED from another pin on the +5 V supply. Is it clear how the rows and columns of pin sockets are connected in the left and right protoboards? You should have two LEDs lit.
3. The three protoboards in the center of the ELVIS unit contain more pin sockets arranged in rows and columns. Using your wires to map out the connections between pins in each of the sections of the protoboard (i.e. connect the 5V DC to socket A60 on your prototyping board and use a different wire to connect your LED to A59. Does the LED light up? What if you connect the LED wire to B60 instead?). Use colored pens or pencils to label/illustrate these connections. Only one or two rows/columns need to be drawn for each section.



Warning: If you are confused about any of the concepts introduced so far, ask for clarification from an instructor or TA. We will be using ELVIS every week, so it is critical that you understand the system to *save time in future weeks*.

Part 2: DC Analysis of Simple Circuits


Introduction

In this section of the lab, you will use the ELVIS system to analyze the direct current (DC) response of different circuits. The following instructions will suggest methods you can follow in your analysis. You are free to experiment with other options within ELVIS to perform the requested measurements; if in doubt, ask a TA during lab for assistance.

For reference, when we say “measure the voltage (or potential) between point A and point B”, we mean “measure the potential *difference* between point A and point B”. If we just say “measure the voltage at point B”, we mean “measure the potential difference between point B and ground” (which we define as 0 volts).

Voltage Divider

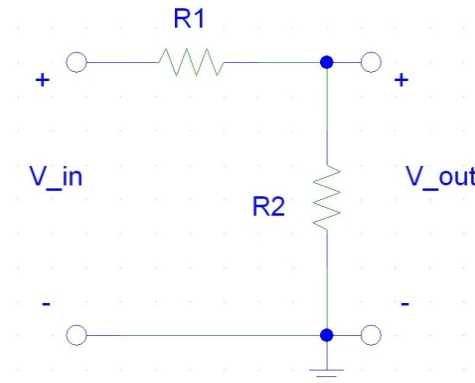The figure below depicts a voltage divider.



1. What is the relationship between the input voltage, V_{in} , and the output voltage, V_{out} , in terms of $R1$ and $R2$?
2. In general, such relationships between input and output signals are to be referred to as transfer functions, because they describe the transfer of information, in this case a voltage, from the input to the output of a device. We can represent the transfer function, H , by the relationship:


$$V_{out} = H \times V_{in}$$

3. Assume that we want $H = 0.5$ for the voltage divider. If $R2 = 100 \, \Omega$, what should $R1$ be?
4. Construct a voltage divider on the ELVIS protoboard using the values of $R1$ and $R2$ from part 3 above. Do not apply V_{IN} yet.
5. Now apply a DC input to the voltage divider (V_{IN}), and measure the output (V_{OUT}). One way to apply a DC input is to use the virtual instrument function generator from Part 1. To do this, connect a wire to the variable power supply and set it to 2V. This produces a constant output voltage; check this with the virtual oscilloscope. Use a wire to apply this power supply output to your voltage divider at the $V_{IN} +$ point. (Recall from the last section how the signals are delivered to the protoboard). Measure the output voltage (the voltage across $R2$). You can use either the digital oscilloscope included in ELVIS, or the handheld FLUKE multimeters. Ask the TAs about how to use the multimeters.
6. What output do you expect? What output do you see? *If your output doesn't quite match what you expected to see, why do you think this is the case? If your output does match what you expect, can you speculate why it wouldn't? Where are inaccuracies most likely to come from?*

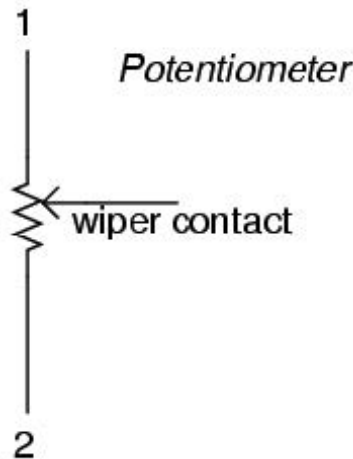
7. Rearrange your voltage divider to obtain a transfer function $H = 0.3$. Input a 3Vp-p sinusoidal signal into your voltage divider. Show the TA your results. Describe the results you obtain.

Using a variable resistor (potentiometer)

Potentiometers provide varying degrees of resistance that can be set by turning a manual knob. The movable element (wiper) makes contact with a resistive strip of material closer to or further away from each one of the two terminals, therefore varying the resistance across. In this section, we will learn how potentiometers work and how to wire them.



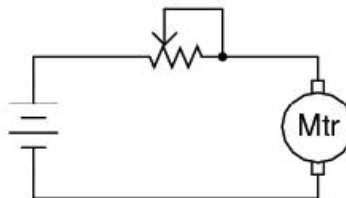1. Using 5VDC as your input, create the following circuit (rheostat) using a 200 W potentiometer. *Note: Ignore the load for now.*




2. Connect the potentiometer using the middle and one of the side leads (wire the unused terminal to the middle lead or wiper).
3. Adjust the resistance by turning the screw on the pot.
4. Using an external DMM to adjust the resistance across the two connected terminals of your potentiometer, and the ELVIS oscilloscope to measure the voltage across your potentiometer, calculate current output across your 'load.' Record your findings in the following table. *Note: turn off your protoboard power when measuring the resistance/adjusting the pot.*
5. What would happen if the resistance between your connected terminals is decreased until it reads 0Ω ?
6. Explain how this circuit is working and possible applications of this setup. *Hint: if you are still not sure about what you are seeing, connect an external DMM to measure the current as you adjust your pot.*

Resistance (Ω)	Voltage across the pot (V)	Current (I)
10		
50		
100		
150		
200		

Back to Voltage Dividers

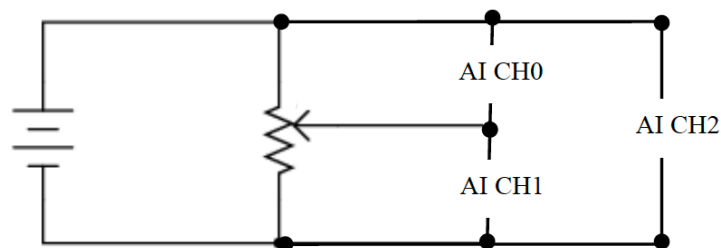
- Using a 5VDC as your input, create the following circuit using a 200 Ω potentiometer.




- Connect the potentiometer using all 3 terminals (5V and ground should be connected to the outer terminals).
- Adjust the resistance by turning the screw on the pot (measure using an external DMM).
- Using the virtual NI ELVIS II oscilloscope, describe the behavior you observe in Ch0, Ch1 and Ch2 as you turn the knob on the potentiometer.
- Explain how this circuit is working and possible applications of this setup.

Wheatstone Bridge

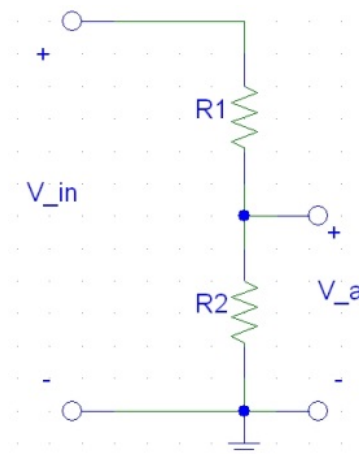Modifying the topology of the divider from part I ($H=0.5$; $R_2=100\Omega$) and re-labeling “V_out” as “V_a”, we have:



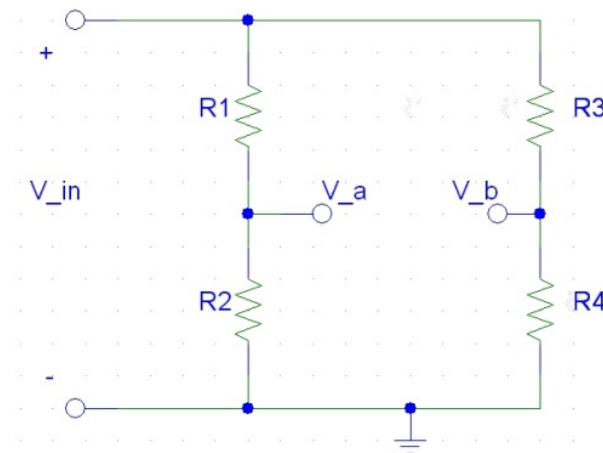We can add another, identical voltage divider to this circuit (do not build until step 3)



where $R1 = R3$, and $R2 = R4$.

1. Using the values of $R1$ and $R2$ from part (I), what do you expect the value of V_a to be in terms of V_{in} ? What about V_b ?
2. If you consider your output, " V_{out} ", to be the difference between V_a and V_b , what would you expect this output to be?
3. Construct the Wheatstone bridge by building off of your circuit from 1. However, use a strain gage instead of $R4$. Strain gages are wafer like resistors whose resistance changes in response to being stretched or compressed. The gage is a two-terminal device that is mounted onto a surface and allows you to measure strain in the material.
4. Apply a DC voltage across the V_{in} terminals (you can use the same input from part (I), and measure the potential at V_a . Measure V_b . Are they the same? If not, why not?
5. With no strain applied to the gage, we require $V_a = V_b$, which would result in $V_{out} = 0$. i.e. a balanced bridge. This is necessary to be able to accurately detect changes in strain when resistance changes in any one arm of the bridge. To do this, we can substitute a potentiometer and balance the bridge. Replace $R2$ with a 200Ω pot (use rheostat configuration from above). Balance the bridge by measuring V_{out} and adjust the pot resistance until $V_{out} = 0$.
6. Now that you have balanced the bridge, gently bend the material. You don't want to create a permanent deformation or break it – so please be gentle. What do you see? How does the circuit output vary in response to compression and tension? Qualitatively, how sensitive is the strain gauge?
7. Use the oscilloscope to record some of your observations (a second or two will suffice).
8. How does the relative change in resistance of the gage depend on the applied strain? How would the output voltage of the bridge relate to the strain? Why does it make sense to have the baseline $V_{out} = 0$?