

OIA Lab 1: In Class Assignment

BIOE 385 Bioinstrumentation Laboratory

Print a copy of this packet and bring it to lab!

Student Name: _____ **Total Grade:** /20

Student Name: _____ **Total Grade:** /20

Student Name: _____ **Total Grade:** /20

Have the Instructor or Teaching Assistant initial that you have demonstrated successful completion of each task where designated.

Part 1: ELVIS Orientation

Introduction to ELVIS

- Generate 500 Hz signal using the manual controls
 - Vertical scale? _____
 - Timebase that results in a few cycles of your signal displayed _____
- Does your signal appear stable on oscilloscope screen?
TA check: _____

Triggers

- What happens to your signal?
- You are now looking at your triggered signal. Experiment by adjusting the amplitude and frequency controls on the ELVIS unit. Change the slope, level and horizontal positions. How do these changes affect the triggered signal? Describe how you think the trigger is working.


- Select Run Once under Acquisition Mode on the Oscilloscope screen. Describe the difference between this option and using a trigger signal.

- The previous section used the function generator built into the ELVIS unit. Now generate a signal using the virtual instrument function generator.
 - Adjust your oscilloscope display to show 5 cycles starting and ending at the highest point (signal should look like: VVVVV). Each cycle should cover 2 squares vertically and 2 squares horizontally. Write down the values you used to achieve this.

 - Adjust the DC offset of your signal and describe what happens.
 - Show your signal (described above) to the TA.
TA check: _____

Introduction to the ELVIS Prototyping board

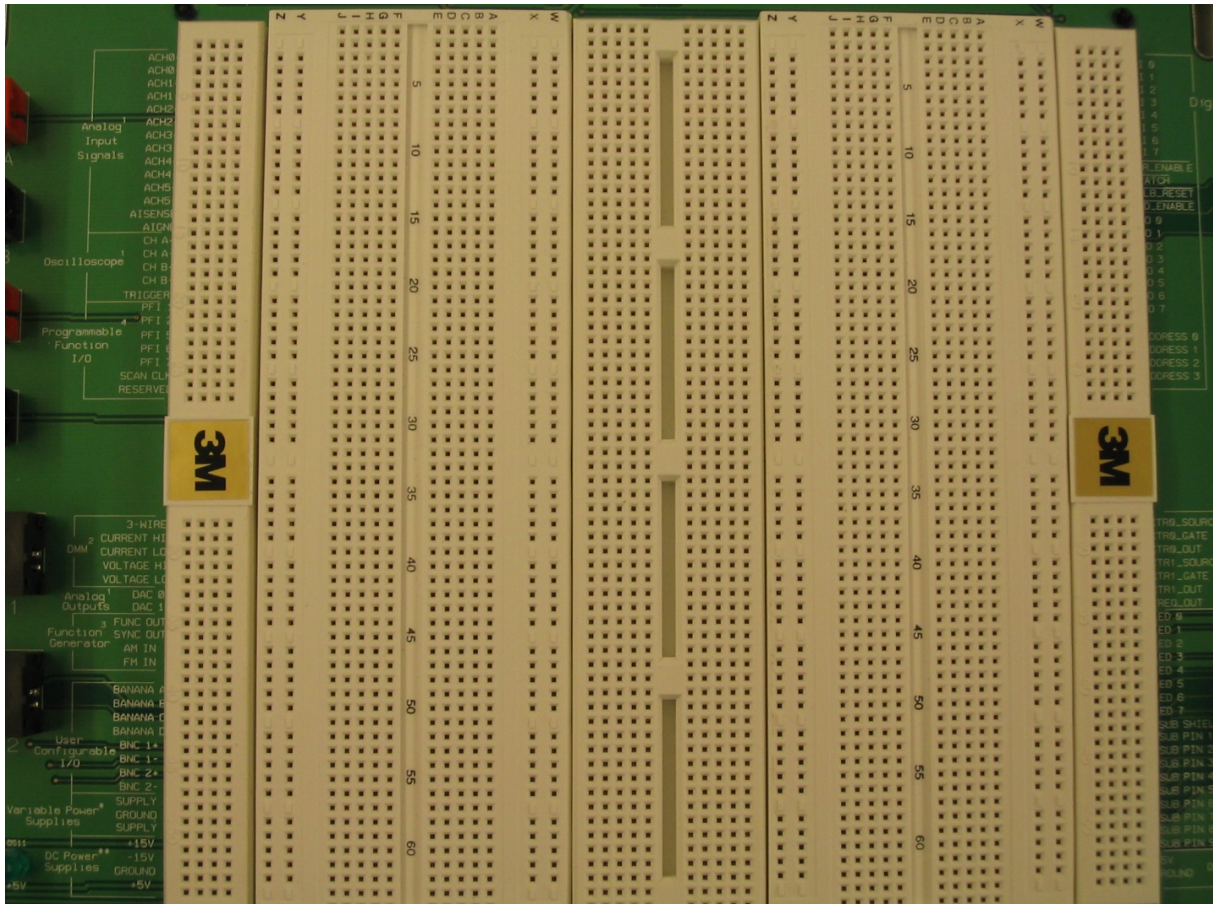- You should have two LEDs lit.
- The three protoboards in the center of the ELVIS unit contain more pin sockets arranged in rows and columns. Using your wires and LEDs on the protoboard to map out the connections between pins in each of the sections of the protoboard. Use colored pens or pencils to label/illustrate these connections.



TA check: _____

Part 2: DC Analysis of Simple Circuits

Voltage Divider

- What is the relationship between the input voltage, V_{in} , and the output voltage, V_{out} , in terms of $R1$ and $R2$?
- Assume that we want $H = 0.5$ for the voltage divider. If $R2 = 100\ \Omega$, what should $R1$ be?
- Construct a voltage divider on the ELVIS protoboard using the values of $R1$ and $R2$ from part 3 above. Do not apply V_{IN} yet.
TA check: _____
- What output do you expect? What output do you see? *If your output doesn't quite match what you expected to see, why do you think this is the case? If your output does match what you expect, can you speculate why it wouldn't? Where are inaccuracies most likely to come from?*
- Rearrange your voltage divider to obtain a transfer function $H = 0.3$. Input a sinusoidal signal into your voltage divider. Show the TA your results. Describe the results you obtain.
TA check: _____

Variable Resistor

- Using an external DMM to adjust the resistance across the two connected terminals of your potentiometer, and the ELVIS oscilloscope to measure the voltage across your potentiometer, calculate current output across your 'load'.

Resistance (Ω)	Voltage across the pot (V)	Current (I)
10		
50		
100		
150		
200		

- What would happen if the resistance between your connected terminals is decreased until it reads 0Ω ?
- Explain how this circuit is working and possible applications of this setup. *Hint: if you are still not sure about what you are seeing, connect an external DMM to measure the current as you adjust your pot.*
TA check: _____

Voltage Divider

- Using the virtual NI ELVIS II oscilloscope, describe the behavior you observe in Ch0, Ch1 and Ch2 as you turn the knob on the potentiometer.
- Explain how this circuit is working and possible applications of this setup.
TA check: _____

Wheatstone Bridge

- Using the values of R_1 and R_2 from part (I), what do you expect the value of V_a to be in terms of V_{in} ? What about V_b ?

- If you consider your output, “V_out”, to be the difference between V_a and V_b, what would you expect this output to be?
- Construct the Wheatstone bridge by building off of your circuit from part (I).
TA check: _____
- Apply a DC voltage across the V_in terminals (you can use the same input from part (I)), and measure the potential at V_a. Measure V_b. Are they the same? If not, why not?
- With no strain applied to the gage, we require $V_a = V_b$, which would result in $V_{out} = 0$. i.e. a balanced bridge. This is necessary to be able to accurately detect changes in strain when resistance changes in any one arm of the bridge. To do this, we can substitute a potentiometer and balance the bridge. Replace R2 with a 200 Ω pot (use rheostat configuration from above). Balance the bridge by measuring V_out and adjust the pot resistance until $V_{out} = 0$.
- Now that you have balanced the bridge, gently bend the material. You don't want to create a permanent deformation or break it – so please be gentle. What do you see? How does the circuit output vary in response to compression and tension? Qualitatively, how sensitive is the strain gauge?
- How does the relative change in resistance of the gage depend on the applied strain? How would the output voltage of the bridge relate to the strain? Why does it make sense to have the baseline $V_{out} = 0$?
TA check: _____